

EXPERIMENT – 5

DESIGN AND SIMULATION OF UJT RELAXATION OSCILLATOR USING

LTSPICE

